
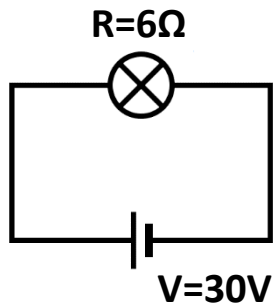
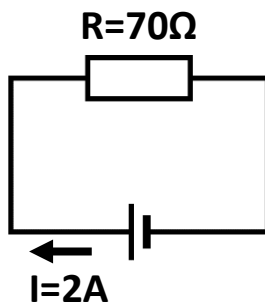
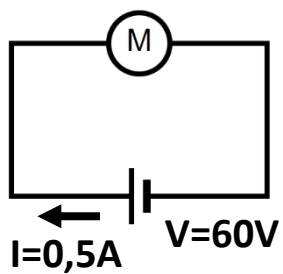
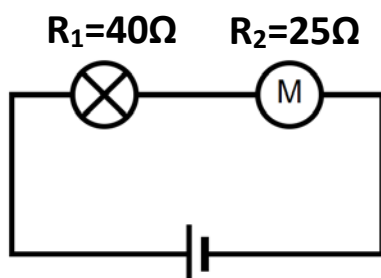



Name: _____ Date: _____

Problem 1: Calculate the intensity of the current of the circuit.**Problem 2:** Calculate the voltage of the battery.**Problem 3:** Calculate the electrical resistance of the motor.**Problem 4:** Calculate the equivalent resistance of the circuit.


Problem 5: Calculate the equivalent resistance of the circuit.

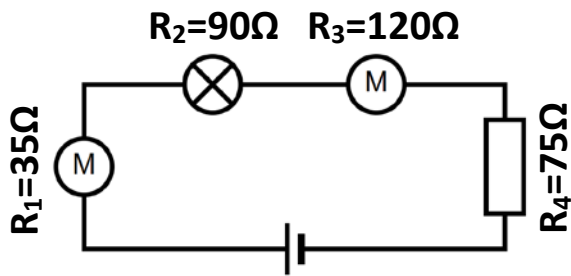


Problem 6: Calculate the equivalent resistance of the circuit.

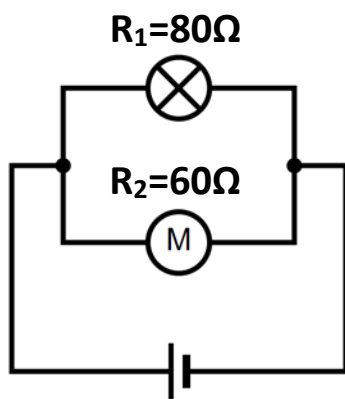


Problem 7: Calculate the equivalent resistance of the circuit.

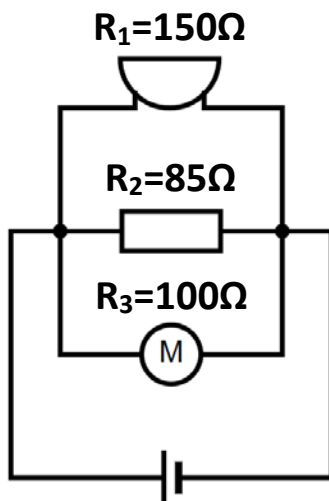


Problem 8: Calculate the intensity of the current that leaves the battery.

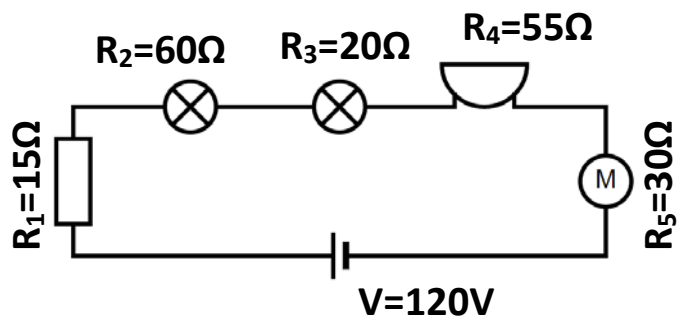

Problem 9: Calculate the intensity of the current that leaves the battery.

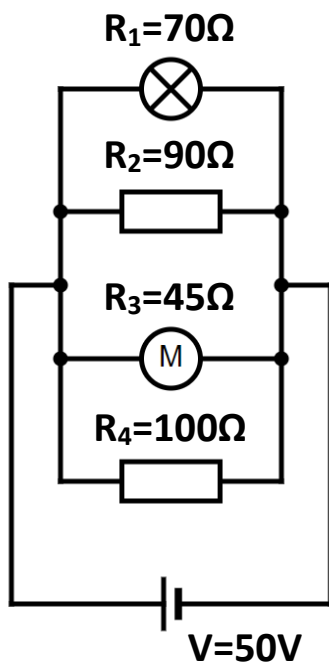

Problem 10: Calculate the voltage of the battery.

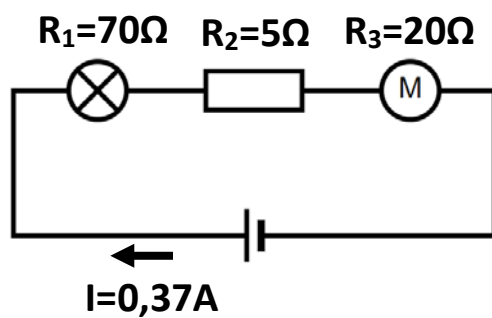

Problem 11: Calculate the voltage of the battery.

